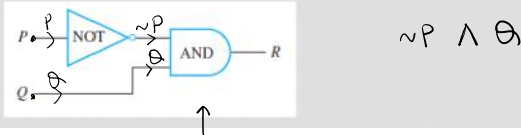


$1 \rightarrow T$
 $0 \rightarrow F$
 Boolean variables (P, Q, \dots) \rightarrow simple statements
 Boolean expressions \rightarrow compound statements
 \sim, \wedge, \vee


	circuit	input-output table																	
NOT		<table border="1"> <thead> <tr> <th>Input</th> <th>Output</th> </tr> <tr> <th>P</th> <th>R</th> </tr> </thead> <tbody> <tr> <td>1</td> <td>0</td> </tr> <tr> <td>0</td> <td>1</td> </tr> </tbody> </table>	Input	Output	P	R	1	0	0	1									
Input	Output																		
P	R																		
1	0																		
0	1																		
AND		<table border="1"> <thead> <tr> <th>Input</th> <th>Output</th> </tr> <tr> <th>P</th> <th>Q</th> <th>R</th> </tr> </thead> <tbody> <tr> <td>1</td> <td>1</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>0</td> </tr> <tr> <td>0</td> <td>1</td> <td>0</td> </tr> <tr> <td>0</td> <td>0</td> <td>0</td> </tr> </tbody> </table>	Input	Output	P	Q	R	1	1	1	1	0	0	0	1	0	0	0	0
Input	Output																		
P	Q	R																	
1	1	1																	
1	0	0																	
0	1	0																	
0	0	0																	
OR		<table border="1"> <thead> <tr> <th>Input</th> <th>Output</th> </tr> <tr> <th>P</th> <th>Q</th> <th>R</th> </tr> </thead> <tbody> <tr> <td>1</td> <td>1</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>0</td> <td>0</td> <td>0</td> </tr> </tbody> </table>	Input	Output	P	Q	R	1	1	1	1	0	1	0	1	1	0	0	0
Input	Output																		
P	Q	R																	
1	1	1																	
1	0	1																	
0	1	1																	
0	0	0																	

1) The Boolean Expression Corresponding to a Circuit


! Combine from left to right..



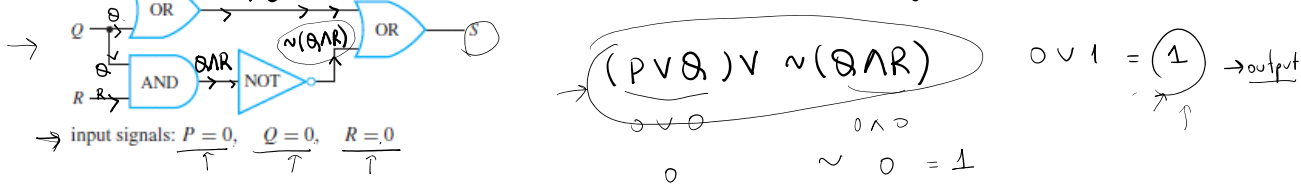4. Write the Boolean exp. correspondingly to circuit.



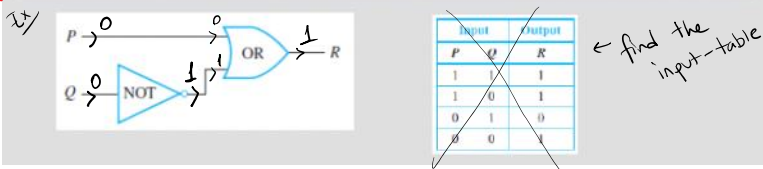
2) Constructing the Input/Output Table for a Circuit



input		output
P	Q	R
→ 1	1	1
→ 1	0	1
→ 0	1	0
→ 0	0	1

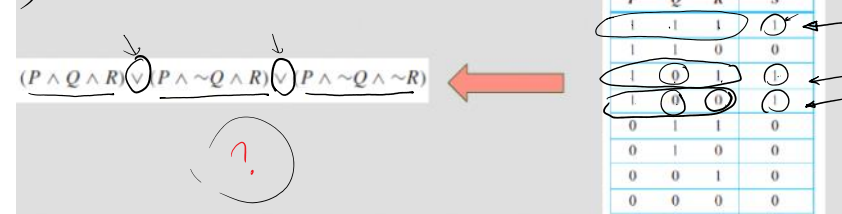
3) The Boolean Expression Corresponding to a ~~circuit~~ input-output table

- Identify the rows where the Output is 1.
- For each such row, construct an AND expression that produces a 1 for the exact combination of input values.
- Use an OR connective at the end.



- $(P \wedge Q \wedge R) \checkmark$
- $(P \wedge \sim Q \wedge R) \checkmark$
- $(P \wedge \sim Q \wedge \sim R) \checkmark$

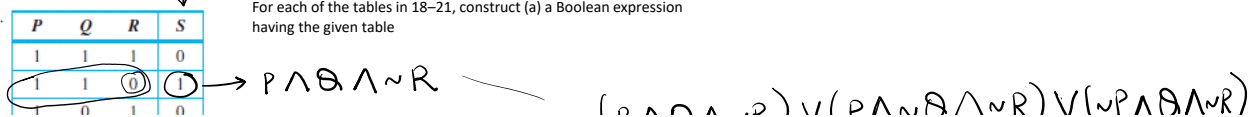19. For each of the tables in 18-21, construct (a) a Boolean expression having the given table



having the given table

P	Q	R	S
1	1	1	0
1	1	0	1
1	0	1	0
1	0	0	1
0	1	1	0
0	1	0	1
0	0	1	0
0	0	0	0


$(1, 1, 0, 1) \rightarrow P \wedge Q \wedge \sim R$
 $(1, 0, 0, 1) \rightarrow P \wedge \sim Q \wedge \sim R$
 $(0, 1, 0, 1) \rightarrow \sim P \wedge Q \wedge \sim R$

$$(P \wedge Q \wedge \sim R) \vee (P \wedge \sim Q \wedge \sim R) \vee (\sim P \wedge Q \wedge \sim R)$$


Finding a Circuit That Corresponds to a Given Boolean Expression

! From outer to the inner; from right to left
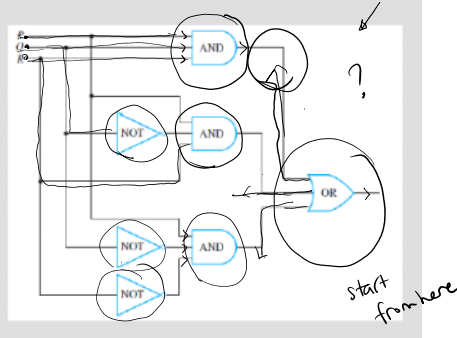
$$(P \wedge Q \wedge R) \vee (P \wedge \sim Q \wedge R) \vee (\sim P \wedge Q \wedge \sim R)$$



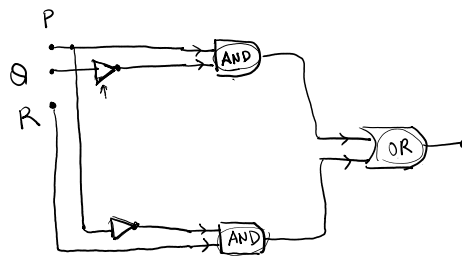17. $(P \wedge \sim Q) \vee (\sim P \wedge R)$



(b) Draw a circuit having the given table as its input/output table.

19.

P	Q	R	S
1	1	1	0
1	1	0	1
1	0	1	0
1	0	0	1
0	1	1	0
0	1	0	1
0	0	1	0
0	0	0	0

black box

a) $(P \wedge Q \wedge \sim R) \vee (P \wedge \sim Q \wedge \sim R) \vee (\sim P \wedge Q \wedge \sim R)$ ✓

